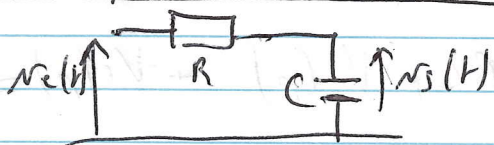


# Filtre passe-bas (1<sup>er</sup> ordre)



$$i = C \frac{dv_s(t)}{dt}$$

$$v_s - v_e = -R \cdot i(t) = -RC \frac{dv_s(t)}{dt}$$

$$\rightarrow \boxed{RC \frac{dv_s(t)}{dt} + v_s(t) = v_e(t)}$$

En Laplace:  $RCp V_s(p) + V_s(p) = V_e(p)$

$$H(p) = \frac{V_s(p)}{V_e(p)} = \frac{1}{1 + RCp}$$

$$\boxed{H(p) = \frac{1}{1 + \tau p}} \quad \text{avec } \tau = RC$$

Discretisons l'équation temporelle.

On pose  $\frac{dv_s(t)}{dt} \approx \frac{v_s[k] - v_s[k-1]}{T_e}$

donc  $RC \frac{v_s[k] - v_s[k-1]}{T_e} + v_s[k] = v_e[k]$

donc  $v_s[k] \left(1 + \frac{RC}{T_e}\right) = \frac{RC}{T_e} v_s[k-1] + v_e[k]$

"  $\left(\frac{T_e + RC}{T_e}\right)$  " "

$$v_s[k] = \frac{RC}{T_e + RC} v_s[k-1] + \frac{T_e}{T_e + RC} v_e[k]$$

on pose  $d = \frac{RC}{T_e + RC}$   $1-d = \frac{T_e + RC - RC}{T_e + RC} = \frac{T_e}{T_e + RC}$

alors  $\boxed{v_s[k] = d \cdot v_s[k-1] + (1-d) \cdot v_e[k]}$

$d = \frac{\tau}{T_e + \tau}$  , si  $T_e \gg \tau \Rightarrow d$  proche de 0  
 , si  $T_e \ll \tau \Rightarrow d$  proche de 1

donc  $0 < d < 1$

## Etudiions dans l'espace z:

$$v_s[k] = d \cdot v_s[k-1] + (1-d) \cdot v_e[k]$$

$$Z\{v_s[k]\} = V_s(z)$$

$$Z\{v_e[k]\} = V_e(z)$$

$$Z\{v_s[k-1]\} = z^{-1} \cdot V_s(z)$$

Rappel  $Z\{y[k]\} = \sum_{k=0}^{\infty} y[k] \cdot z^{-k}$

$$Z\{y[k-1]\} = \sum y[k-1] \cdot z^{-k}$$

$$= \underbrace{y[-1] \cdot z^0}_{k=0} + \underbrace{y[0] \cdot z^1}_{k=1}$$

$$+ y[1] \cdot z^2 + \dots$$

$y[-1] = 0$  car signal causal donc

$$Z\{y[k-1]\} = 0 + y[0] \cdot z^{-1} + y[1] \cdot z^{-2} + \dots$$

$$= y[0] \cdot z^0 \cdot z^{-1} + y[1] \cdot z^1 \cdot z^{-2} + \dots$$

$$= z^{-1} \cdot (y[0] \cdot z^0 + y[1] \cdot z^1)$$

$$\boxed{Z\{y[k-1]\} = z^{-1} \cdot Z\{y[k]\}}$$

$$V_s(z) = d \cdot z^{-1} V_s(z) + (1-d) \cdot V_e(z)$$

$$\boxed{H(z) = \frac{V_s(z)}{V_e(z)} = \frac{1-d}{1-d \cdot z^{-1}}}$$